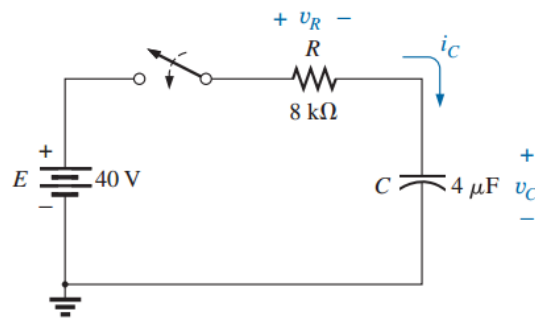


Question 1

**EXAMPLE 10.6** For the circuit in Fig. 10.38:

- Find the mathematical expression for the transient behavior of  $v_C$ ,  $i_C$ , and  $v_R$  if the switch is closed at  $t = 0$  s.
- Plot the waveform of  $v_C$  versus the time constant of the network.
- Plot the waveform of  $v_C$  versus time.
- Plot the waveforms of  $i_C$  and  $v_R$  versus the time constant of the network.
- What is the value of  $v_C$  at  $t = 20$  ms?
- On a practical basis, how much time must pass before we can assume that the charging phase has passed?
- When the charging phase has passed, how much charge is sitting on the plates?

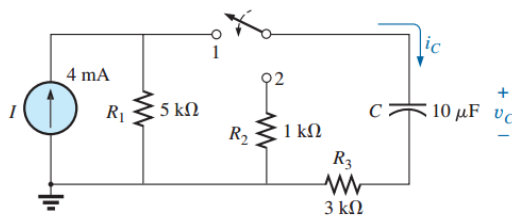


**FIG. 10.38**  
Transient network for Example 10.6.

Question 2

**EXAMPLE 10.9** For the network in Fig. 10.49:

- Find the mathematical expression for the transient behavior of the voltage across the capacitor if the switch is thrown into position 1 at  $t = 0$  s.
- Find the mathematical expression for the transient behavior of the voltage across the capacitor if the switch is moved to position 2 at  $t = 1\tau$ .




**FIG. 10.49**  
Network to be analyzed in Example 10.9.

- Plot the resulting waveform for the voltage  $v_C$  as determined by parts (a) and (b).
- Repeat parts (a)–(c) for the current  $i_C$ .

### Question 3

**EXAMPLE 10.11** For the network in Fig. 10.60:

- Find the mathematical expression for the transient behavior of the voltage  $v_C$  and the current  $i_C$  following the closing of the switch (position 1 at  $t = 0$  s).
- Find the mathematical expression for the voltage  $v_C$  and the current  $i_C$  as a function of time if the switch is thrown into position 2 at  $t = 9$  ms.
- Draw the resultant waveforms of parts (a) and (b) on the same time axis.

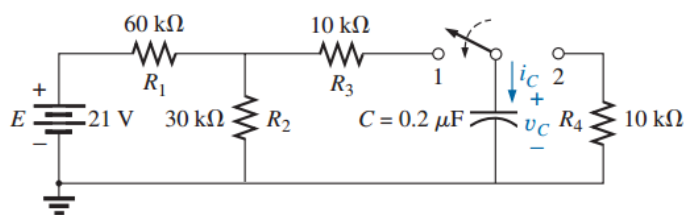


**FIG. 10.60**  
Example 10.11.

### Question 4

**EXAMPLE 11.7** Switch  $S_1$  in Fig. 11.51 has been closed for a long time. At  $t = 0$  s,  $S_1$  is opened at the same instant that  $S_2$  is closed to avoid an interruption in current through the coil.

- Find the initial current through the coil. Pay particular attention to its direction.

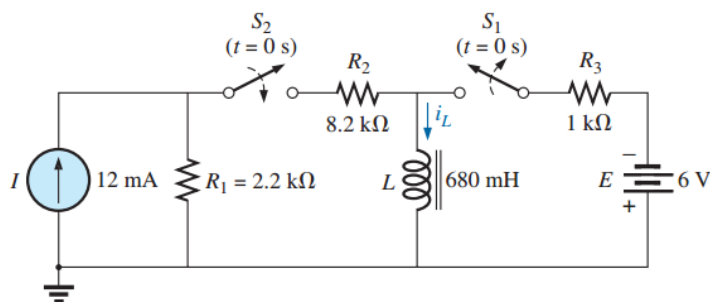

**FIG. 11.51**  
Example 11.7.

- Find the mathematical expression for the current  $i_L$  following the closing of switch  $S_2$ .
- Sketch the waveform for  $i_L$ .