

Question 1 (10-23)

For the network of Fig. 10.83:

- Find the mathematical expression for the voltage across the capacitor after the switch is thrown into position 1.
- Repeat part (a) for the current  $i_C$ .
- Find the mathematical expressions for the voltage  $v_C$  and current  $i_C$  if the switch is thrown into position 2 at a time equal to five time constants of the charging circuit.
- Plot the waveforms of  $v_C$  and  $i_C$  for a period of time extending from  $t = 0$  to  $t = 30 \mu\text{s}$ .

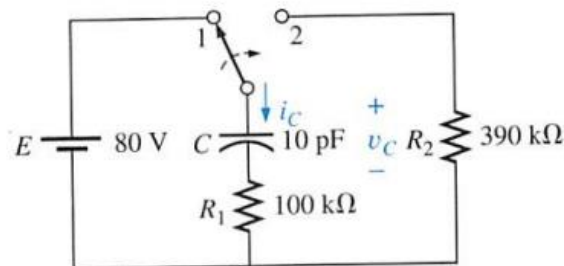


FIG. 10.83  
Problem 23.

Question 2 (10-27)

- \*27. The capacitor of Fig. 10.87 is initially charged to 12 V with the polarity shown.
- Find the mathematical expressions for the voltage  $v_C$  and the current  $i_C$  when the switch is closed.
  - Sketch the waveforms for  $v_C$  and  $i_C$ .

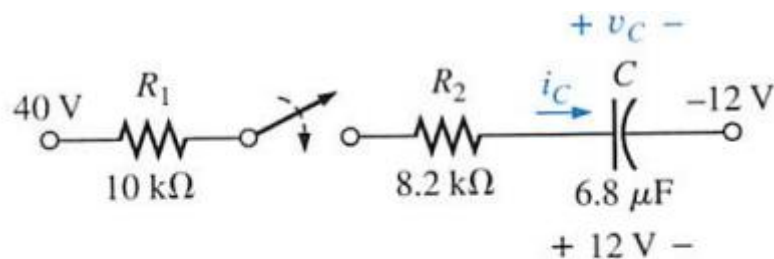


FIG. 10.87  
Problem 27.

Question 3 (10-41)

41. Find the waveform for the average current if the voltage across a  $0.06\text{-}\mu\text{F}$  capacitor is as shown in Fig. 10.99.

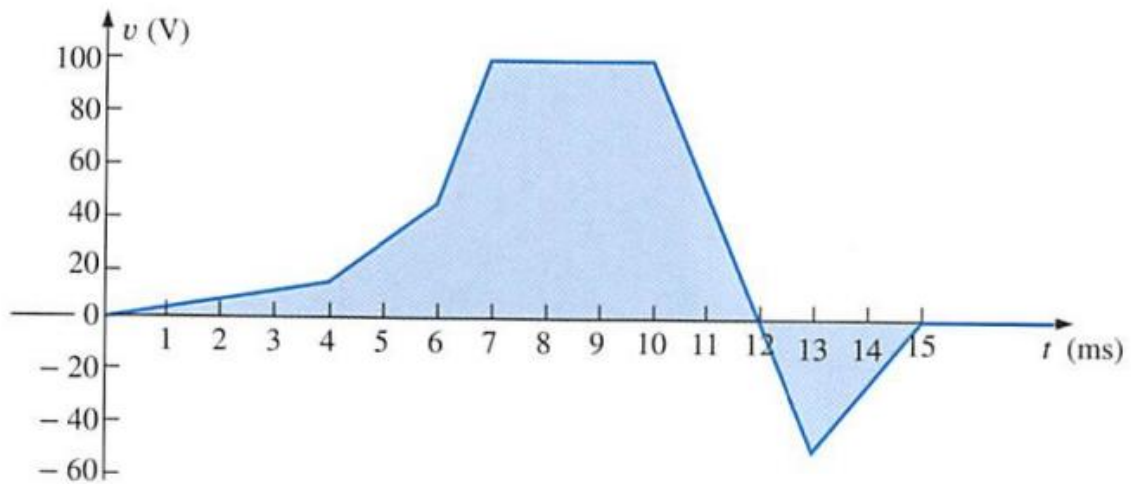


FIG. 10.99  
Problem 41.

Question 4 (12-10)

10. Sketch the waveform for the voltage induced across a  $0.2\text{-H}$  coil if the current through the coil is as shown in Fig. 12.65.

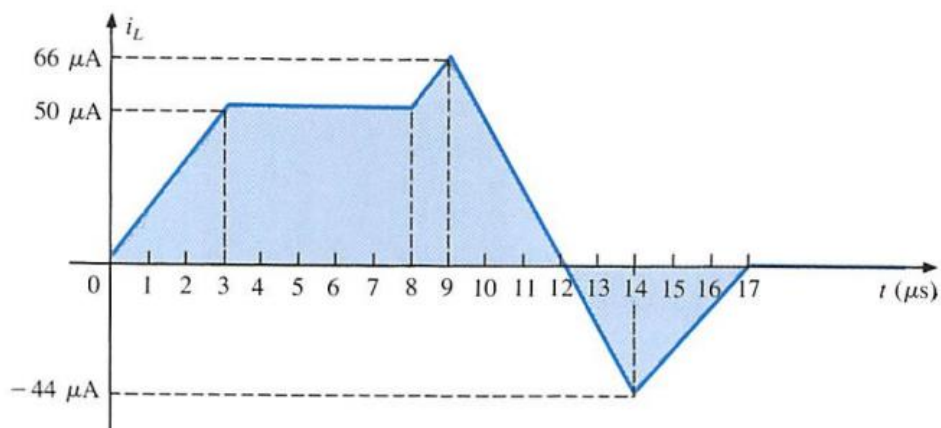


FIG. 12.65  
Problem 10.

Question 5 (12-15)

\*15. For the network of Fig. 12.70:

- Write the mathematical expression for the current  $i_L$  and the voltage  $v_L$  following the closing of the switch.
- Determine the mathematical expressions for  $i_L$  and  $v_L$  if the switch is opened after a period of five time constants has passed.
- Sketch the waveforms of  $i_L$  and  $v_L$  for the time periods defined by parts (a) and (b).
- Sketch the waveform for the voltage across  $R_2$  for the same period of time encompassed by  $i_L$  and  $v_L$ . Take careful note of the defined polarities and directions of Fig. 12.70.


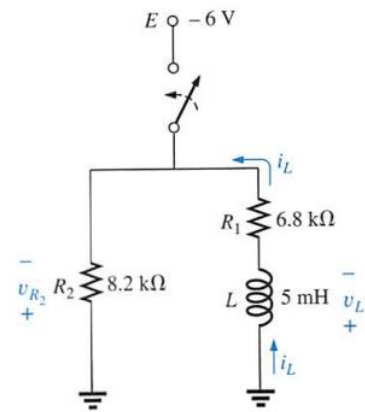


FIG. 12.70  
Problem 15.

Solution


Question 1

23. a.  $\tau = R_1 C = (10^5 \Omega)(10 \text{ pF}) = 1 \mu\text{s}$   
 $v_C = 80(1 - e^{-t/1 \times 10^{-6}})$
- b.  $i_C = \frac{80 \text{ V}}{100 \text{ k}\Omega} e^{-t/\tau} = 0.8 \times 10^{-3} e^{-t/1 \times 10^{-6}}$
- c.  $\tau' = R' C = (490 \text{ k}\Omega)(10 \text{ pF}) = 4.9 \mu\text{s}$   
 $v_C = 80 e^{-t/\tau'} = 80 e^{-t/4.9 \times 10^{-6}}$   
 $i_C = \frac{80 \text{ V}}{490 \text{ k}\Omega} e^{-t/\tau'} = 0.163 \times 10^{-3} e^{-t/4.9 \times 10^{-6}}$
- d.

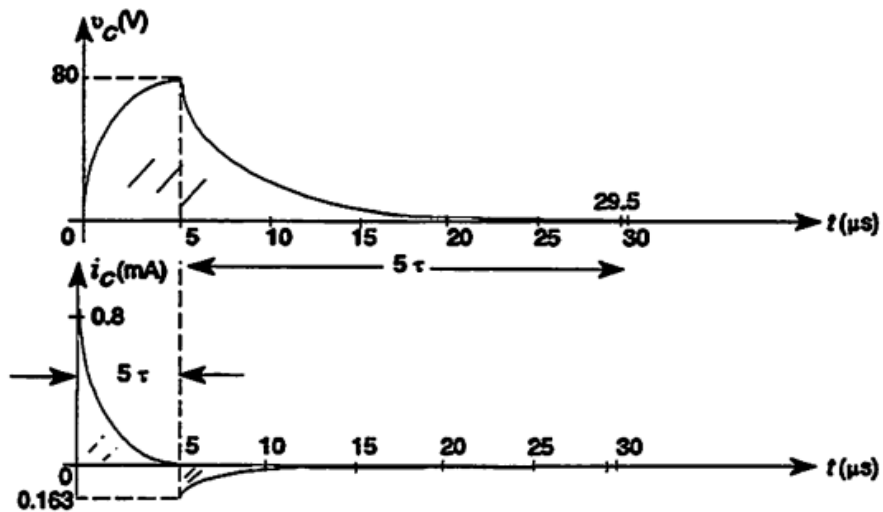

Question 2

27. a.

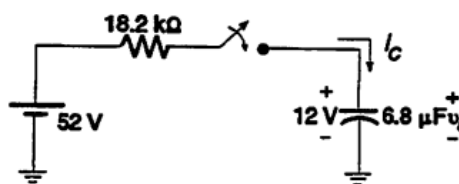

$$\tau = RC = (18.2 \text{ k}\Omega)(6.8 \mu\text{F}) = 123.8 \text{ ms}$$

$$v_C = V_f + (V_i - V_f)e^{-t/\tau}$$

$$= 52 \text{ V} + (12 \text{ V} - 52 \text{ V})e^{-t/123.8 \text{ ms}}$$


$$v_C = 52 \text{ V} - 40 \text{ V}e^{-t/123.8 \text{ ms}}$$

$$v_R(0+) = 52 \text{ V} - 12 \text{ V} = 40 \text{ V}$$

$$i_C = \frac{40 \text{ V}}{18.2 \text{ k}\Omega} e^{-t/123.8 \text{ ms}}$$

$$= 2.198 \text{ mA}e^{-t/123.8 \text{ ms}}$$

- b.

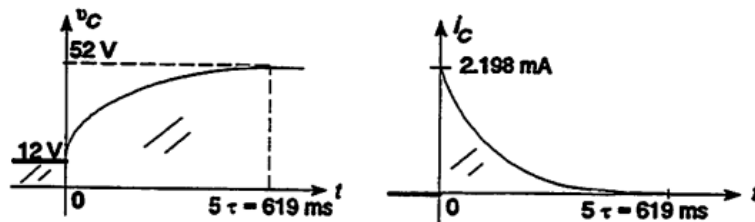

Question 3

$$41. \quad i_C = C \frac{\Delta V}{\Delta t}; \quad i_C = 0.06 \times 10^{-6} \frac{\Delta V}{\Delta t}$$

$$0 - 4 \text{ ms: } i_C = 0.06 \times 10^{-6} \left[ \frac{20 \text{ V}}{4 \text{ ms}} \right] = 0.3 \text{ mA}$$


$$4 - 6 \text{ ms: } i_C = 0.06 \times 10^{-6} \left[ \frac{30 \text{ V}}{2 \text{ ms}} \right] = 0.9 \text{ mA}$$

$$6 - 7 \text{ ms: } i_C = 0.06 \times 10^{-6} \left[ \frac{50 \text{ V}}{1 \text{ ms}} \right] = 3 \text{ mA}$$

$$7 - 10 \text{ ms: } i_C = 0 \text{ mA}$$

$$10 - 13 \text{ ms: } i_C = -0.06 \times 10^{-6} \left[ \frac{160 \text{ V}}{3 \text{ ms}} \right] = -3.2 \text{ mA}$$

$$13 - 15 \text{ ms: } i_C = 0.06 \times 10^{-6} \left[ \frac{60 \text{ V}}{2 \text{ ms}} \right] = 1.8 \text{ mA}$$

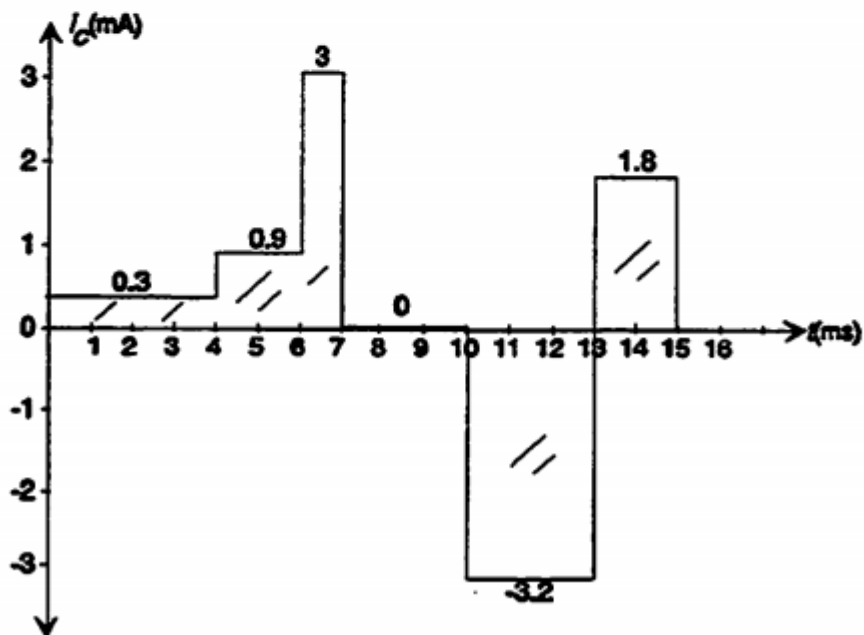

Question 4

$$10. \quad e = L \frac{\Delta i}{\Delta t} = (0.2 \text{ H}) \frac{\Delta i}{\Delta t}$$


$$0 - 3 \mu\text{s}: e = (0.2 \text{ H}) \left[ \frac{50 \mu\text{A}}{3 \mu\text{s}} \right] = 3.33 \text{ V}$$

$$3 - 8 \mu\text{s}: e = (0.2 \text{ H})(0) = 0 \text{ V}$$

$$8 - 9 \mu\text{s}: e = (0.2 \text{ H}) \left[ \frac{16 \mu\text{A}}{1 \mu\text{s}} \right] = 3.2 \text{ V}$$


$$9 - 14 \mu\text{s}: e = -(0.2 \text{ H}) \left[ \frac{100 \mu\text{A}}{5 \mu\text{s}} \right] = -4 \text{ V}$$

$$14 - 17 \mu\text{s}: e = (0.2 \text{ H}) \left[ \frac{44 \mu\text{A}}{3 \mu\text{s}} \right] = 2.93 \text{ V}$$

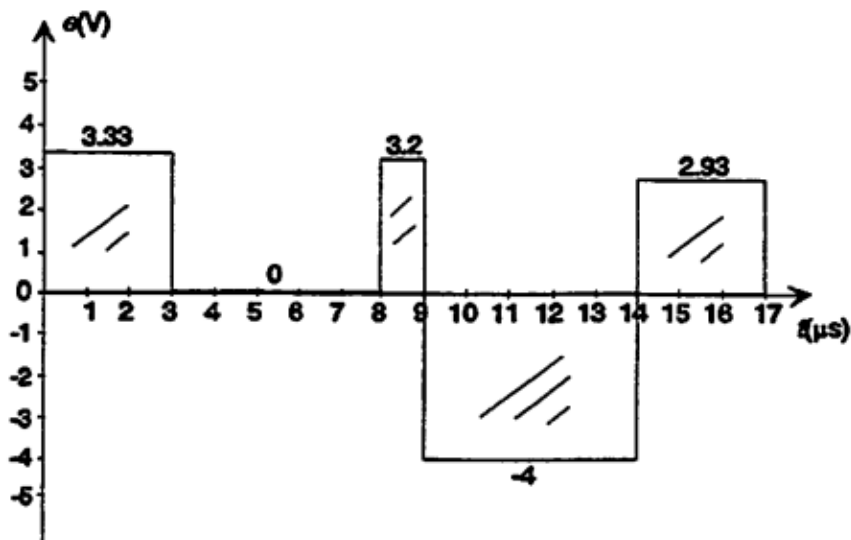


Question 5

15. a.

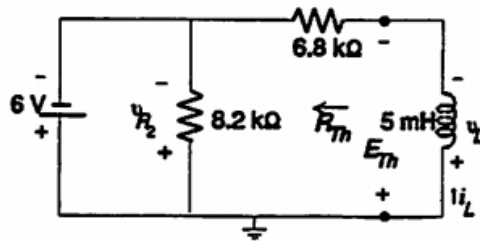

$$R_{Th} = 6.8 \text{ k}\Omega$$

$$E_{Th} = 6 \text{ V}$$

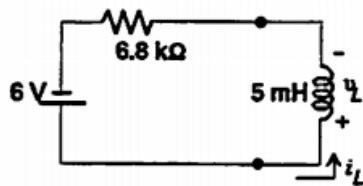


$$\tau = \frac{L}{R} = \frac{5 \text{ mH}}{6.8 \text{ k}\Omega} = 0.735 \mu\text{s}$$

$$i_L = \frac{E}{R}(1 - e^{-t/\tau}) = \frac{6 \text{ V}}{6.8 \text{ k}\Omega}(1 - e^{-t/\tau}) = 0.882 \times 10^{-3}(1 - e^{-t/0.735 \mu\text{s}})$$

$$v_L = Ee^{-t/\tau} = 6e^{-t/0.735 \mu\text{s}}$$

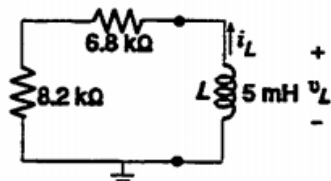b. Assume steady state and  $I_L = 0.882 \text{ mA}$



$$\tau' = \frac{L}{R} = \frac{5 \text{ mH}}{15 \text{ k}\Omega} = 0.333 \mu\text{s}$$

$$i_L = I_m e^{-t/\tau'} = 0.882 \times 10^{-3} e^{-t/0.333 \mu\text{s}}$$



$$v_L = -V_m e^{-t/\tau'}$$

↑ compared to defined polarity of Fig. 12.62.

$$V_m = I_m R = (0.882 \text{ mA})(15 \text{ k}\Omega) = 13.23 \text{ V}$$

$$v_L = -13.23 e^{-t/0.333 \mu\text{s}}$$

c.

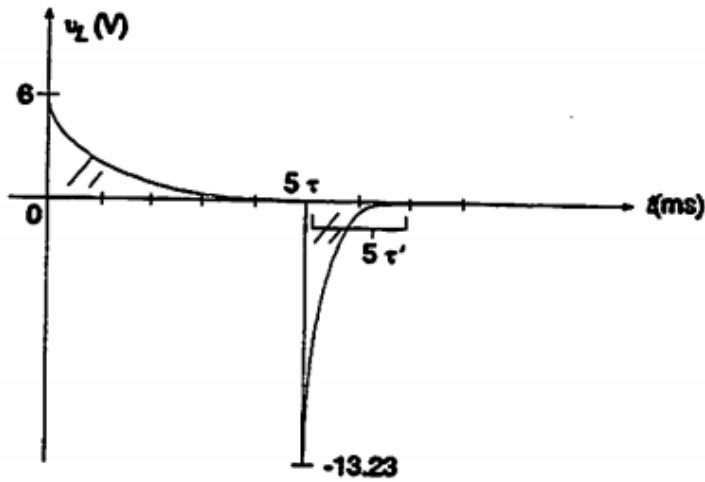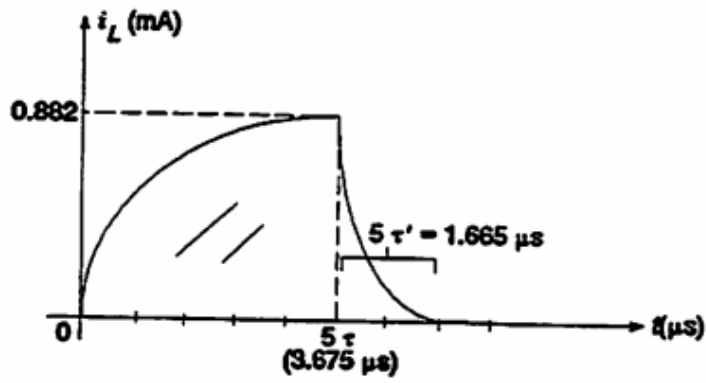

d. For polarity of Fig. 12.62:

$$V_{R_2 \max} = I_m R_2 = (0.882 \text{ mA})(8.2 \text{ k}\Omega) = 7.23 \text{ V}$$

