

Question 1 (10-23)

For the network of Fig. 10.83:

- Find the mathematical expression for the voltage across the capacitor after the switch is thrown into position 1.
- Repeat part (a) for the current  $i_C$ .
- Find the mathematical expressions for the voltage  $v_C$  and current  $i_C$  if the switch is thrown into position 2 at a time equal to five time constants of the charging circuit.
- Plot the waveforms of  $v_C$  and  $i_C$  for a period of time extending from  $t = 0$  to  $t = 30 \mu\text{s}$ .

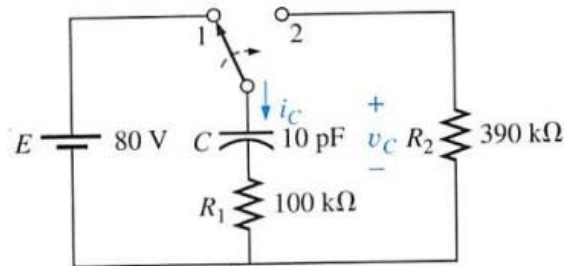


FIG. 10.83

Problem 23.

Question 2 (10-27)

\*27. The capacitor of Fig. 10.87 is initially charged to 12 V with the polarity shown.

- Find the mathematical expressions for the voltage  $v_C$  and the current  $i_C$  when the switch is closed.
- Sketch the waveforms for  $v_C$  and  $i_C$ .

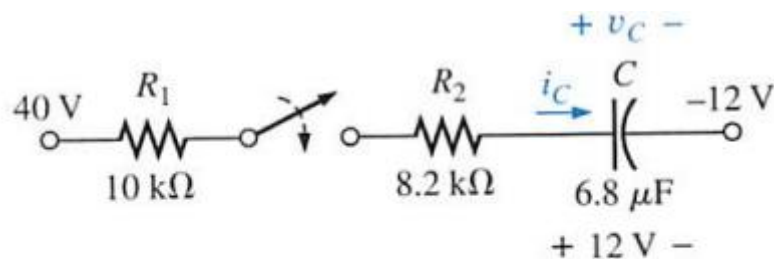


FIG. 10.87

Problem 27.

Question 3 (10-41)

41. Find the waveform for the average current if the voltage across a  $0.06\text{-}\mu\text{F}$  capacitor is as shown in Fig. 10.99.

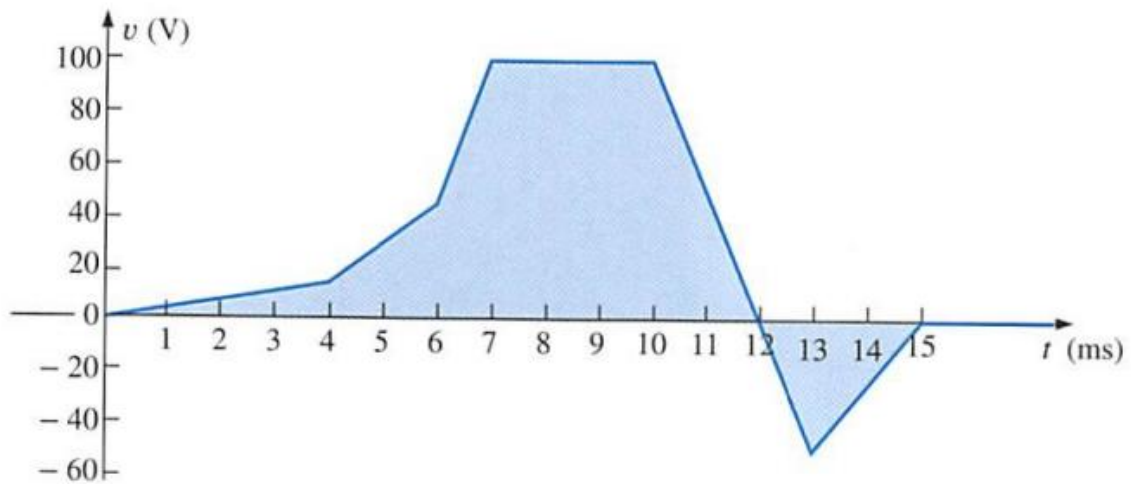


FIG. 10.99  
Problem 41.

Question 4 (12-10)

10. Sketch the waveform for the voltage induced across a  $0.2\text{-H}$  coil if the current through the coil is as shown in Fig. 12.65.

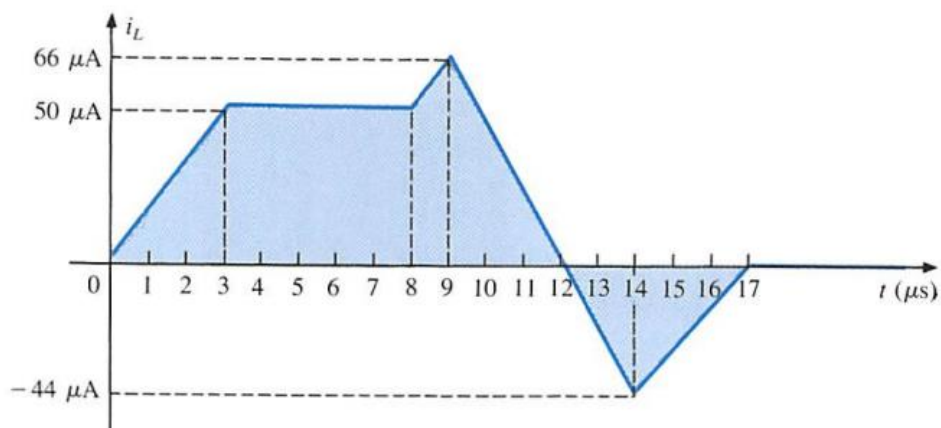


FIG. 12.65  
Problem 10.

Question 5 (12-15)

\*15. For the network of Fig. 12.70:

- Write the mathematical expression for the current  $i_L$  and the voltage  $v_L$  following the closing of the switch.
- Determine the mathematical expressions for  $i_L$  and  $v_L$  if the switch is opened after a period of five time constants has passed.
- Sketch the waveforms of  $i_L$  and  $v_L$  for the time periods defined by parts (a) and (b).
- Sketch the waveform for the voltage across  $R_2$  for the same period of time encompassed by  $i_L$  and  $v_L$ . Take careful note of the defined polarities and directions of Fig. 12.70.

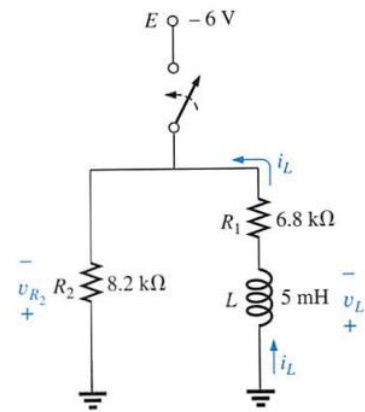


FIG. 12.70  
Problem 15.