

Tutorial - 1-02-g

Question 0

Find the relationship between dc supply power and ac supply power, by using the setup shown below:


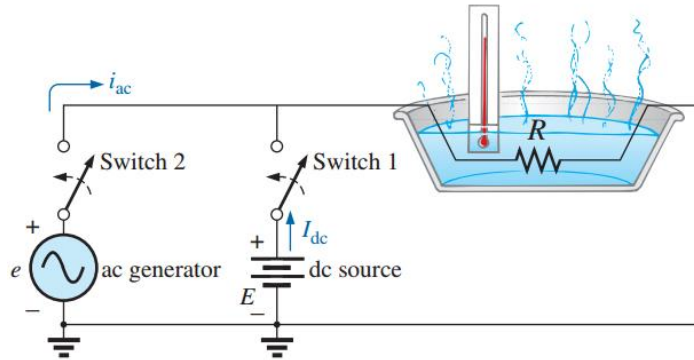


FIG. 13.59


An experimental setup to establish a relationship between dc and ac quantities.

Question 1 (13-39)

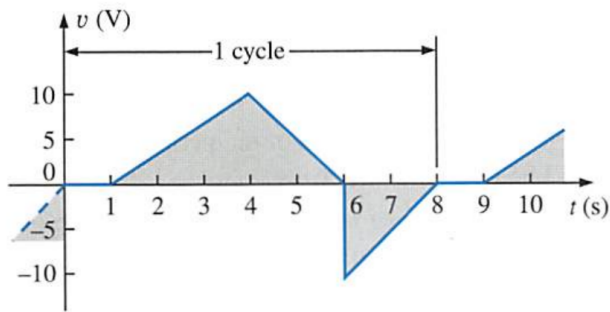39. Find the average value of the periodic waveforms of Fig. 13.92 over one full cycle.



(a)

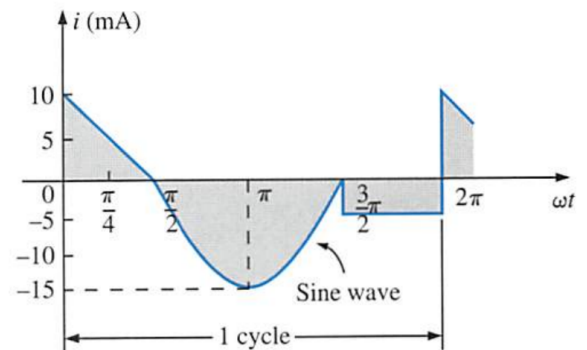


(b)

FIG. 13.92

Problem 39.

Question 2 (13-45)


45. Find the effective value of the periodic waveform of Fig. 13.96 over one full cycle.

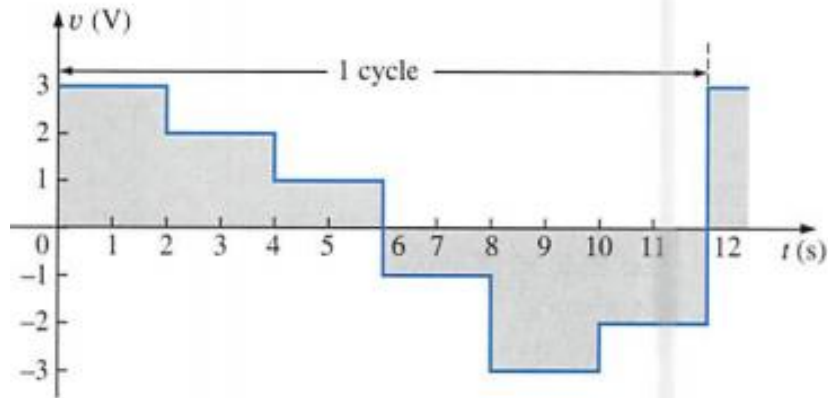

**FIG. 13.96**  
Problem 45.

Question 3 (14-35)

35. In Fig. 14.75,  $e = 100 \sin(157t + 30^\circ)$ .
- Find the sinusoidal expression for  $i$ .
  - Find the value of the inductance  $L$ .
  - Find the average power loss by the inductor.

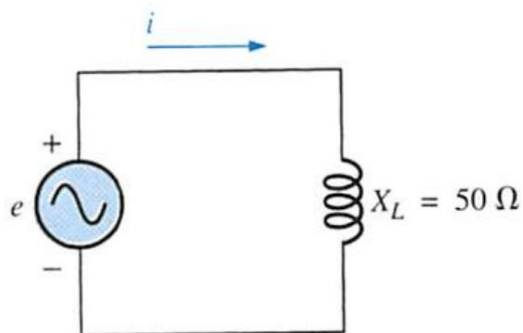

**FIG. 14.75**

Question 4 (14-47)

47. a. Determine a solution for  $x$  and  $y$  if

$$(x + j4) + (3x + jy) - j7 = 16 \angle 0^\circ$$

- b. Determine  $x$  if

$$(10 \angle 20^\circ)(x \angle -60^\circ) = 30.64 - j25.72$$

- c. Determine a solution for  $x$  and  $y$  if

$$(5x + j10)(2 - jy) = 90 - j70$$

- d. Determine  $\theta$  if

$$\frac{80 \angle 0^\circ}{20 \angle \theta} = 3.464 - j2$$


Question 5 (14-52)

52. Find the sinusoidal expression for the applied voltage  $e$  for the system of Fig. 14.81 if

$$v_a = 60 \sin(\omega t + 30^\circ)$$

$$v_b = 30 \sin(\omega t - 30^\circ)$$

$$v_c = 40 \sin(\omega t + 120^\circ)$$

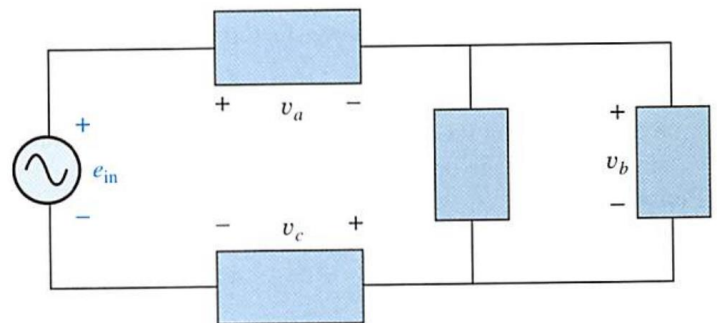

**FIG. 14.81**  
Problem 52.

SOLUTION

Q0

The power delivered by the ac supply at any instant of time is

$$P_{ac} = (i_{ac})^2 R = (I_m \sin \omega t)^2 R = (I_m^2 \sin^2 \omega t) R$$

However,

$$\sin^2 \omega t = \frac{1}{2} (1 - \cos 2\omega t) \quad (\text{trigonometric identity})$$

Therefore,

$$P_{ac} = I_m^2 \left[ \frac{1}{2} (1 - \cos 2\omega t) \right] R$$

and

$$P_{ac} = \frac{I_m^2 R}{2} - \frac{I_m^2 R}{2} \cos 2\omega t \quad (13.30)$$

Equating the average power delivered by the ac generator to that delivered by the dc source,

$$P_{av(ac)} = P_{dc}$$

$$\frac{I_m^2 R}{2} = I_{dc}^2 R$$

and

$$I_{dc} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

which, in words, states that

***the equivalent dc value of a sinusoidal current or voltage is  $1/\sqrt{2}$  or 0.707 of its peak value.***

Q1

$$39. \quad a. \quad G = \frac{\frac{1}{2}(3 \text{ s})(10 \text{ V}) + \frac{1}{2}(2 \text{ s})(10 \text{ V}) - \frac{1}{2}(2 \text{ s})(10 \text{ V})}{8 \text{ s}}$$

$$= \frac{15 \text{ V} + 10 \text{ V} - 10 \text{ V}}{8} = 1.875 \text{ V}$$

$$b. \quad G = \frac{\frac{1}{2} \left[ \frac{\pi}{2} \right] (10 \text{ mA}) - 2(15 \text{ mA}) - \frac{\pi}{2} (5 \text{ mA})}{2\pi}$$

$$= \frac{2.5\pi \text{ mA} - 30 \text{ mA} - 2.5\pi \text{ mA}}{2\pi}$$

$$= \frac{-30 \text{ mA}}{2\pi} = -4.775 \text{ mA}$$

Q2

$$45. \quad V_{\text{eff}} = \sqrt{\frac{(3 \text{ V})^2(2 \text{ s}) + (2 \text{ V})^2(2 \text{ s}) + (1 \text{ V})^2(2 \text{ s}) + (-1 \text{ V})^2(2 \text{ s}) + (-3 \text{ V})^2(2 \text{ s}) + (-2 \text{ V})^2(2 \text{ s})}{12 \text{ s}}}$$

$$= +2.16 \text{ V}$$

Q3

$$35. \quad a. \quad I_m = \frac{V_m}{X_L} = \frac{100 \text{ V}}{50 \Omega} = 2 \text{ A}, \quad i = 2 \sin(157t - 60^\circ)$$

$$b. \quad X_L = \frac{V_m}{I_m} = \frac{100 \text{ V}}{2 \text{ A}} = 50 \Omega, \quad L = \frac{X_L}{\omega} = \frac{50 \Omega}{157 \text{ rad/s}} = 318.47 \text{ mH}$$

$$c. \quad L \Rightarrow 0 \text{ W}$$

Q4

$$47. \quad a. \quad \begin{array}{l} x + j4 + 3x + jy - j7 = 16 \\ (x + 3x) + j(4 + y - 7) = 16 + j0 \\ x + 3x = 16 \qquad \qquad \qquad 4 + y - 7 = 0 \\ 4x = 16 \qquad \qquad \qquad y = +7 - 4 \\ x = 4 \qquad \qquad \qquad y = 3 \end{array}$$

$$b. \quad \begin{array}{l} (10 \angle 20^\circ)(x \angle -60^\circ) = 30.64 - j25.72 \\ 10x \angle -40^\circ = 40 \angle -40^\circ \\ 10x = 40 \\ x = 4 \end{array}$$

c.  $\frac{5x + j10}{2 - jy}$

$$10x + j20 - j5xy - j^2 10y = 90 - j70$$

$$(10x + 10y) + j(20 - 5xy) = 90 - j70$$

$$10x + 10y = 90$$

$$x + y = 9$$

$$x = 9 - y \Rightarrow$$

$$20 - 5xy = -70$$

$$20 - 5(9 - y)y = -70$$

$$5y(9 - y) = 90$$

$$y^2 - 9y + 18 = 0$$

$$y = \frac{-(-9) \pm \sqrt{(-9)^2 - 4(1)(18)}}{2}$$

$$y = \frac{9 \pm 3}{2} = 6, 3$$

For  $y = 6, x = 3$

$y = 3, x = 6$

$(x = 3, y = 6)$  or  $(x = 6, y = 3)$

d.  $\frac{80 \angle 0^\circ}{40 \angle \theta} = 4 \angle -\theta = 3.464 - j2 = 4 \angle -30^\circ$   
 $\theta = 30^\circ$

Q5

52.

$$e = v_a + v_b + v_c$$

$$= 60 \text{ V } \angle 30^\circ + 30 \text{ V } \angle -30^\circ + 40 \text{ V } \angle 120^\circ$$

$$= (51.96 + j30) + (25.98 - j15) + (-20 + j34.64)$$

$$= 57.94 + j49.64$$

$$= 76.297 \text{ V } \angle 40.59^\circ$$

and  $e = 76.297 \sin(\omega t + 40.59^\circ)$