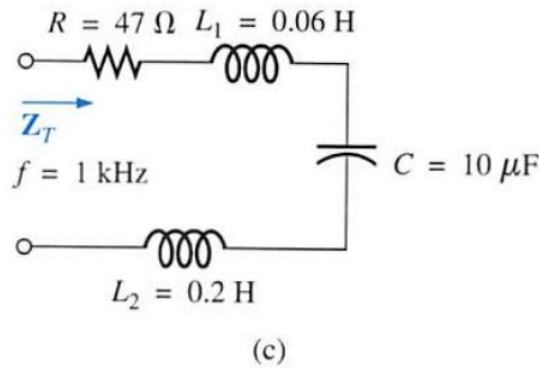


**Tutorial - 1-02-h**

**Question 1 (15-3-5-c)**


Calculate the total impedance of the circuits of Fig. 15.121. Express your answer in rectangular and polar forms, and draw the impedance diagram.



**Question 2 (15-4-17)**

\*17. For the circuit of Fig. 15.133:

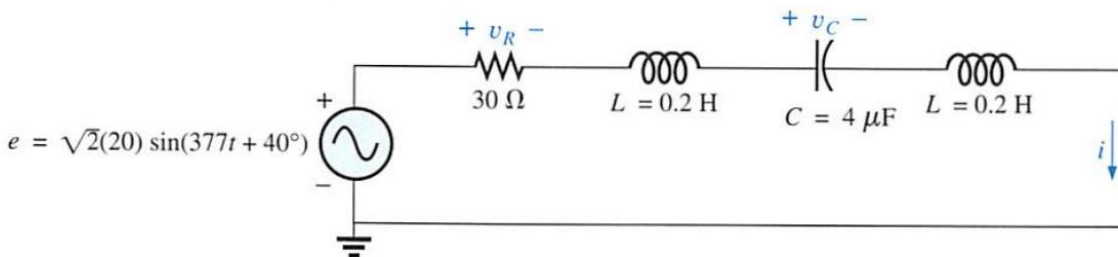- a. Determine  $\mathbf{I}$ ,  $\mathbf{V}_R$ , and  $\mathbf{V}_C$  in phasor form.
- b. Calculate the total power factor, and indicate whether it is leading or lagging.


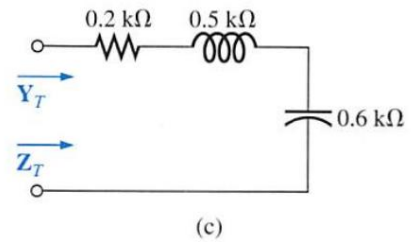
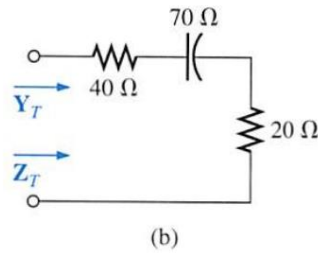


**FIG. 15.133**

- c. Calculate the average power delivered to the circuit.
- d. Draw the impedance diagram.
- e. Draw the phasor diagram of the voltages  $\mathbf{E}$ ,  $\mathbf{V}_R$ , and  $\mathbf{V}_C$ , and the current  $\mathbf{I}$ .
- f. Find the voltages  $\mathbf{V}_R$  and  $\mathbf{V}_C$  using the voltage divider rule, and compare them with the results of part (a) above.
- g. Draw the equivalent series circuit of the above as far as the total impedance and the current  $i$  are concerned.

Question 3 (15-7-25)

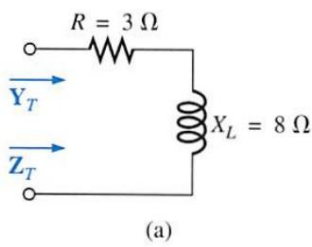25. Find the total admittance and impedance of the circuits of Fig. 15.139. Identify the values of conductance and susceptance, and draw the admittance diagram.



Question 4 (16-2-7)

- \*7. For the network of Fig. 16.42:
- Find the current  $I_1$ .
  - Find the voltage  $V_1$ .
  - Calculate the average power delivered to the network.

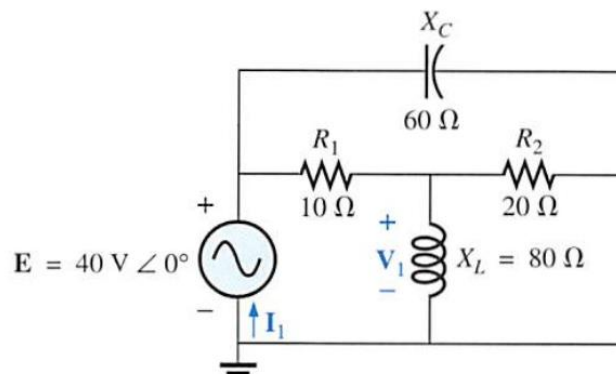


FIG. 16.42

Question 5 (16-2-10)

- \*10. For the network of Fig. 16.45:
- Find the total impedance  $Z_T$  and the admittance  $Y_T$ .
  - Find the source current  $I_s$  in phasor form.
  - Find the currents  $I_1$  and  $I_2$  in phasor form.
  - Find the voltages  $V_1$  and  $V_{ab}$  in phasor form.
  - Find the average power delivered to the network.
  - Find the power factor of the network, and indicate whether it is leading or lagging.

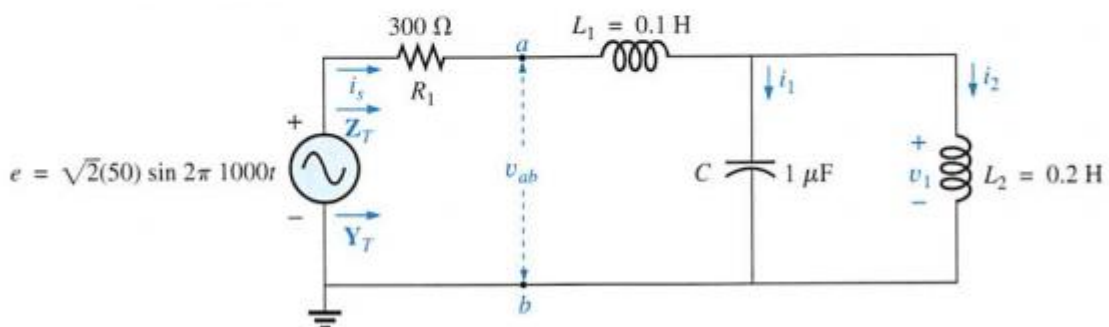


FIG. 16.45