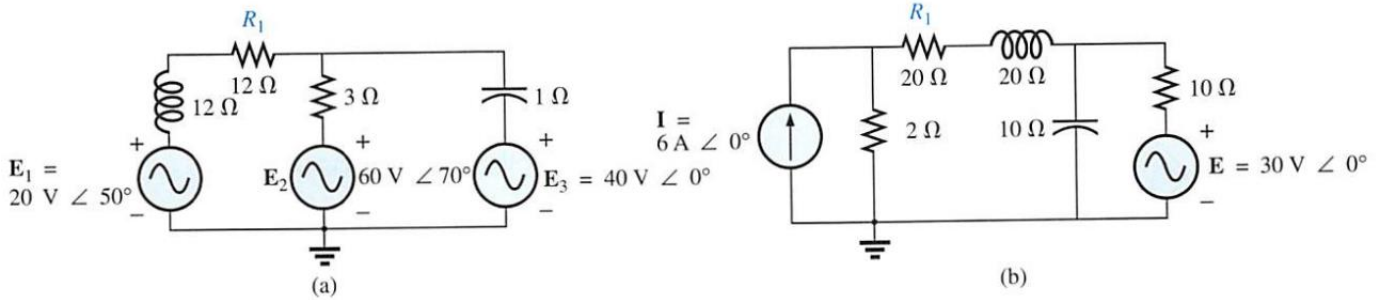


Tutorial - 1-02-h

Question 1 (17-6)

6. Write the mesh equations for the networks of Fig. 17.62. Determine the current through the resistor R_1 .



Question 2 (17-8)

*8. Write the mesh equations for the networks of Fig. 17.64. Determine the current through the resistor R_1 .


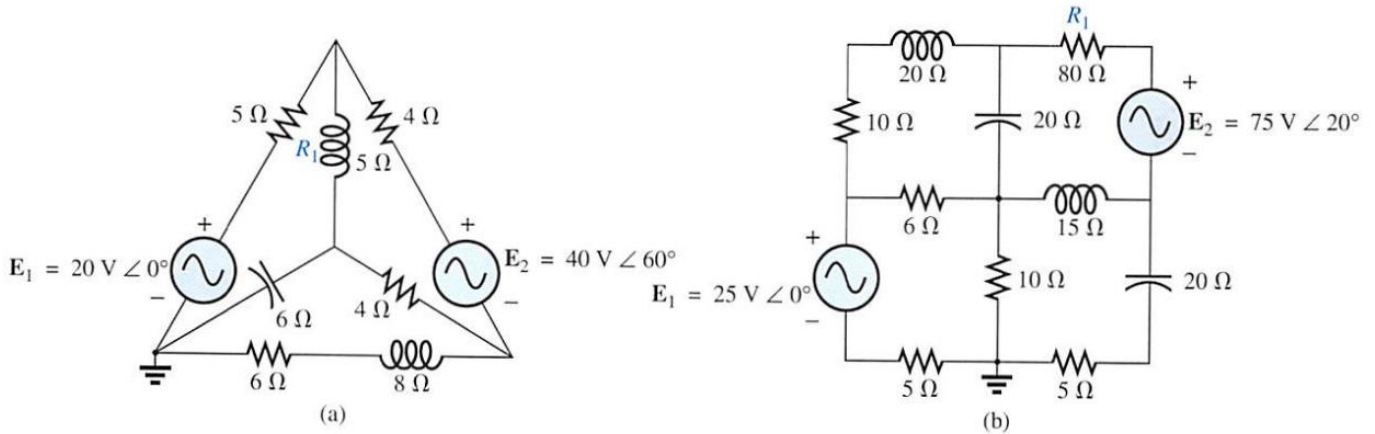


FIG. 17.64

Question 3 (18-13)

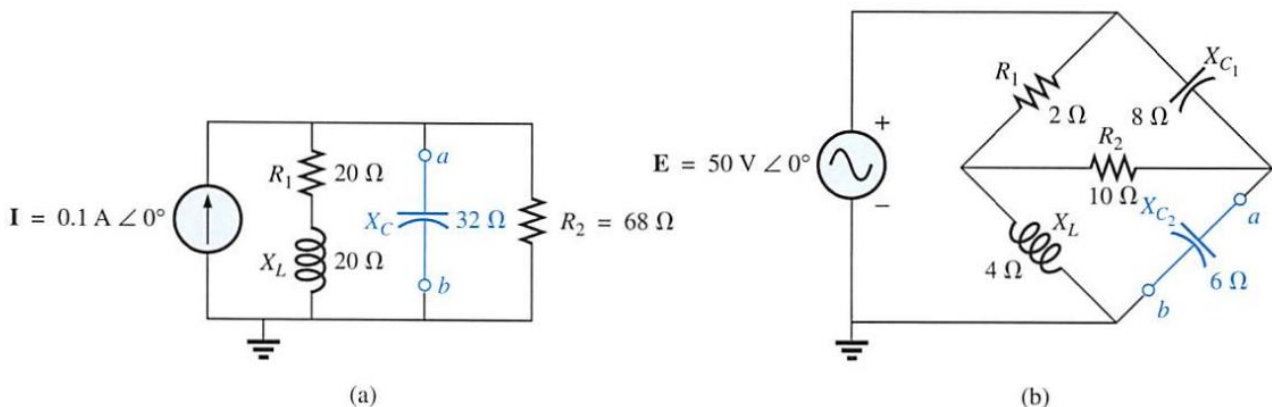
*13. Find the Thévenin equivalent circuit for the portions of the networks of Fig. 18.120 external to the elements between points a and b .



SOLUTION

Q1

6. a.

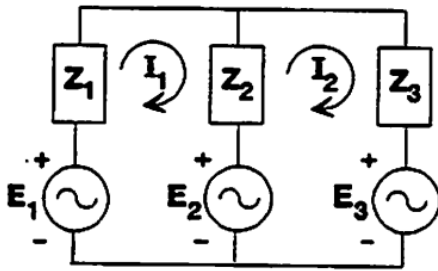

$$\begin{aligned} Z_1 &= 12 \Omega + j12 \Omega = 16.971 \Omega \angle 45^\circ \\ Z_2 &= 3 \Omega \angle 0^\circ \\ Z_3 &= -j1 \Omega \\ E_1 &= 20 \text{ V } \angle 50^\circ \\ E_2 &= 60 \text{ V } \angle 70^\circ \\ E_3 &= 40 \text{ V } \angle 0^\circ \end{aligned}$$


$$\begin{aligned} I_1[Z_1 + Z_2] - Z_2 I_2 &= E_1 - E_2 \\ I_2[Z_2 + Z_3] - Z_2 I_1 &= E_2 - E_3 \end{aligned}$$

$$\begin{aligned} (Z_1 + Z_2)I_1 - Z_2 I_2 &= E_1 - E_2 \\ -Z_2 I_1 + (Z_2 + Z_3)I_2 &= E_2 - E_3 \end{aligned}$$

Using determinants:

$$I_{R_1} = I_1 = \frac{(E_1 - E_2)(Z_2 + Z_3) + Z_2(E_2 - E_3)}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} = 2.552 \text{ A } \angle 132.72^\circ$$

b.

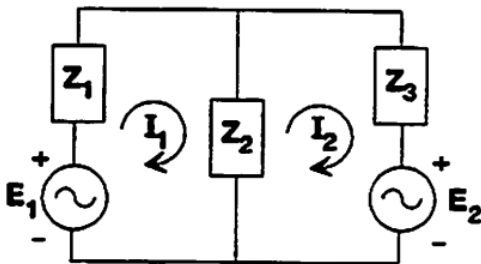

Source conversion:

$$\begin{aligned} E_1 &= IZ = (6 \text{ A } \angle 0^\circ)(2 \Omega \angle 0^\circ) \\ &= 12 \text{ V } \angle 0^\circ \\ Z_1 &= 2 \Omega + 20 \Omega + j20 \Omega = 22 \Omega + j20 \Omega \\ &= 29.732 \Omega \angle 42.274^\circ \\ Z_2 &= -j10 \Omega = 10 \Omega \angle -90^\circ \\ Z_3 &= 10 \Omega \angle 0^\circ \end{aligned}$$


$$\begin{aligned} I_1[Z_1 + Z_2] - Z_2 I_2 &= E_1 \\ I_2[Z_2 + Z_3] - Z_2 I_1 &= -E_2 \end{aligned}$$

$$\begin{aligned} (Z_1 + Z_2)I_1 - Z_2 I_2 &= E_1 \\ -Z_2 I_1 + (Z_2 + Z_3)I_2 &= -E_2 \end{aligned}$$

$$I_{R_1} = I_1 = \frac{E_1(Z_2 + Z_3) - Z_2 E_2}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} = 0.495 \text{ A } \angle 72.255^\circ$$

Q2

8. a.

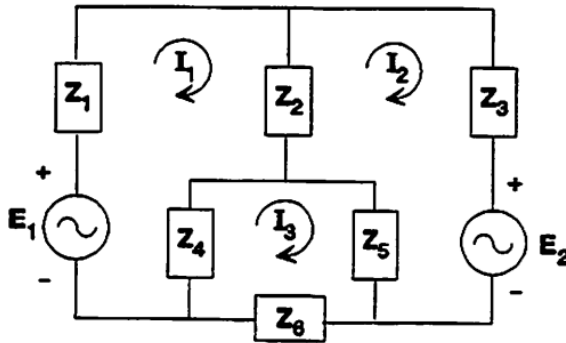

$$\begin{aligned} Z_1 &= 5 \Omega \angle 0^\circ, Z_2 = 5 \Omega \angle 90^\circ \\ Z_3 &= 4 \Omega \angle 0^\circ, Z_4 = 6 \Omega \angle -90^\circ \\ Z_5 &= 4 \Omega \angle 0^\circ, Z_6 = 6 \Omega + j8 \Omega \\ E_1 &= 20 \text{ V } \angle 0^\circ, E_2 = 40 \text{ V } \angle 60^\circ \end{aligned}$$


$$\begin{aligned} I_1(Z_1 + Z_2 + Z_4) - I_2Z_2 - I_3Z_4 &= E_1 \\ I_2(Z_2 + Z_3 + Z_5) - I_1Z_2 - I_3Z_5 &= -E_2 \\ I_3(Z_4 + Z_5 + Z_6) - I_1Z_4 - I_2Z_5 &= 0 \end{aligned}$$

$$\begin{aligned} (Z_1 + Z_2 + Z_4)I_1 & & - Z_2I_2 & & - Z_4I_3 & = E_1 \\ -Z_2I_1 + (Z_2 + Z_3 + Z_5)I_2 & & & & - Z_5I_3 & = -E_2 \\ -Z_4I_1 & & - Z_5I_2 + (Z_4 + Z_5 + Z_6)I_3 & & & = 0 \end{aligned}$$

Using $Z' = Z_1 + Z_2 + Z_4$, $Z'' = Z_2 + Z_3 + Z_5$, $Z''' = Z_4 + Z_5 + Z_6$ and determinants:

$$\begin{aligned} I_{R1} = I_1 &= \frac{E_1(Z''Z''' - Z_5^2) - E_2(Z_2Z''' + Z_4Z_5)}{Z'(Z''Z''' - Z_5^2) - Z_2(Z_2Z''' + Z_4Z_5) - Z_4(Z_2Z_5 + Z_4Z''')} \\ &= 3.04 \text{ A } \angle 169.12^\circ \end{aligned}$$

b.

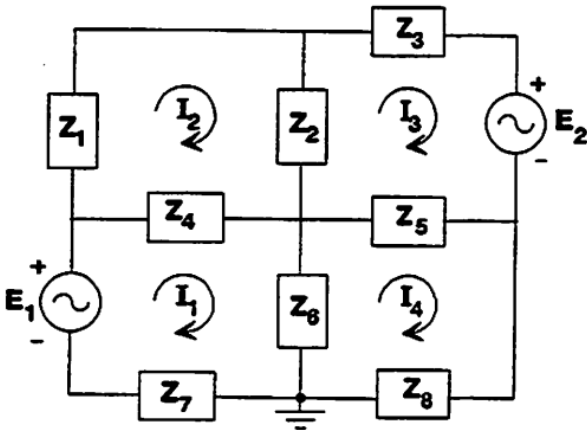

$$\begin{aligned} Z_1 &= 10 \Omega + j20 \Omega & Z_2 &= -j20 \Omega \\ Z_3 &= 80 \Omega \angle 0^\circ & Z_4 &= 6 \Omega \angle 0^\circ \\ Z_5 &= 15 \Omega \angle 90^\circ & Z_6 &= 10 \Omega \angle 0^\circ \\ Z_7 &= 5 \Omega \angle 0^\circ & Z_8 &= 5 \Omega - j20 \Omega \\ E_1 &= 25 \text{ V } \angle 0^\circ & E_2 &= 75 \text{ V } \angle 20^\circ \end{aligned}$$

$$\begin{aligned} I_1(Z_4 + Z_6 + Z_7) - I_2Z_4 - I_4Z_6 &= E_1 \\ I_2(Z_1 + Z_2 + Z_4) - I_1Z_4 - I_3Z_2 &= 0 \\ I_3(Z_2 + Z_3 + Z_5) - I_2Z_2 - I_4Z_5 &= -E_2 \\ I_4(Z_5 + Z_6 + Z_8) - I_1Z_6 - I_3Z_5 &= 0 \end{aligned}$$


$$\begin{aligned} (Z_4 + Z_6 + Z_7)I_1 & & - Z_4I_2 & & + 0 & & - Z_6I_4 & = E_1 \\ -Z_4I_1 + (Z_1 + Z_2 + Z_4)I_2 & & & & - Z_2I_3 & & + 0 & = 0 \\ 0 & & - Z_2I_2 + (Z_2 + Z_3 + Z_5)I_3 & & & & - Z_5I_4 & = -E_2 \\ -Z_6I_1 & & + 0 & & - Z_5I_3 + (Z_5 + Z_6 + Z_7)I_4 & & & = 0 \end{aligned}$$

Applying determinants:

$$I_{R1} = I_{80\Omega} = 0.681 \text{ A } \angle -162.9^\circ$$

Q3

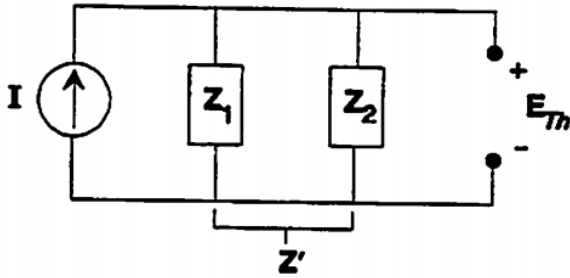- a. From #27. $Z_{Th} = Z_1 \parallel Z_2$
 $Z_{Th} = Z_N = 21.312 \Omega \angle 32.196^\circ$




$$E_{Th} = IZ' = IZ_{Th}$$

$$= (0.1 \text{ A } \angle 0^\circ)(21.312 \Omega \angle 32.196^\circ)$$

$$= 2.131 \text{ V } \angle 32.196^\circ$$

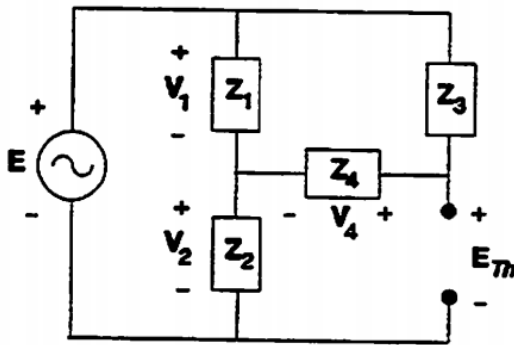- b. From #27. $Z_{Th} = Z_N = 6.813 \Omega \angle -54.228^\circ = 3.983 \Omega - j5.528 \Omega$



$$Z_1 = 2 \Omega \angle 0^\circ, Z_3 = 8 \Omega \angle -90^\circ$$

$$Z_2 = 4 \Omega \angle 90^\circ, Z_4 = 10 \Omega \angle 0^\circ$$

$$E = 50 \text{ V } \angle 0^\circ$$

$$E_{Th} = V_2 + V_4$$

$$V_2 = \frac{Z_2 E}{Z_2 + Z_1 \parallel (Z_3 + Z_4)}$$

$$= \frac{(4 \Omega \angle 90^\circ)(50 \text{ V } \angle 0^\circ)}{+j4 \Omega + 2 \Omega \angle 0^\circ \parallel (10 \Omega - j8 \Omega)}$$

$$= 47.248 \text{ V } \angle 24.7^\circ$$

$$V_1 = E - V_2 = 50 \text{ V } \angle 0^\circ - 47.248 \text{ V } \angle 24.7^\circ = 20.972 \text{ V } \angle -70.285^\circ$$

$$V_4 = \frac{Z_4 V_1}{Z_4 + Z_3} = \frac{(10 \Omega \angle 0^\circ)(20.972 \text{ V } \angle -70.285^\circ)}{10 \Omega - j8 \Omega} = 16.377 \text{ V } \angle -31.625^\circ$$

$$E_{Th} = V_2 + V_4 = 47.248 \text{ V } \angle 24.7^\circ + 16.377 \text{ V } \angle -31.625^\circ$$

$$= (42.925 \text{ V} + j19.743 \text{ V}) + (13.945 \text{ V} - j8.587 \text{ V})$$

$$= 56.870 \text{ V} + j11.156 \text{ V} = 57.954 \text{ V } \angle 11.099^\circ$$