

1-02-k- solution

1. a. $\omega_s = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \text{ H}(16 \mu\text{F})}} = 250 \text{ rad/s}$

$$f_s = \frac{\omega_s}{2\pi} = \frac{250 \text{ rad/s}}{2\pi} = 39.79 \text{ Hz}$$

b. $\omega_s = \frac{1}{\sqrt{(0.5 \text{ H})(0.16 \mu\text{F})}} = 3535.53 \text{ rad/s}$

$$f_s = \frac{\omega_s}{2\pi} = \frac{3535.53 \text{ rad/s}}{2\pi} = 562.7 \text{ Hz}$$

c. $\omega_s = \frac{1}{\sqrt{(0.28 \text{ mH})(7.46 \mu\text{F})}} = 21,880 \text{ rad/s}$

$$f_s = \frac{\omega_s}{2\pi} = \frac{21,880 \text{ rad/s}}{2\pi} = 3482.31 \text{ Hz}$$

2. a. $X_C = 30 \Omega$ b. $Z_{T_s} = 10 \Omega$ c. $I = \frac{E}{Z_{T_s}} = \frac{50 \text{ mV}}{10 \Omega} = 5 \text{ mA}$

d. $V_R = IR = (5 \text{ mA})(10 \Omega) = 50 \text{ mV} = E$

$$V_L = IX_L = (5 \text{ mA})(30 \Omega) = 150 \text{ mV}$$

$$V_C = IX_C = (5 \text{ mA})(30 \Omega) = 150 \text{ mV}$$

$$V_L = V_C$$

e. $Q_s = \frac{X_L}{R} = \frac{30 \Omega}{10 \Omega} = 3 \text{ (low } Q)$

f. $P = I^2R = (5 \text{ mA})^2 10 \Omega = 0.25 \text{ mW}$

3. a. $X_L = 40 \Omega$

b. $I = \frac{E}{Z_{T_s}} = \frac{20 \text{ mV}}{2 \Omega} = 10 \text{ mA}$

c. $V_R = IR = (10 \text{ mA})(2 \Omega) = 20 \text{ mV} = E$
 $V_L = IX_L = (10 \text{ mA})(40 \Omega) = 400 \text{ mV}$
 $V_C = IX_C = (10 \text{ mA})(40 \Omega) = 400 \text{ mV}$
 $V_L = V_C = 20 V_R$

d. $Q_s = \frac{X_L}{R} = \frac{40 \Omega}{2 \Omega} = 20 \text{ (high Q)}$

e. $X_L = 2\pi fL, L = \frac{X_L}{2\pi f} = \frac{40 \Omega}{2\pi(5 \text{ kHz})} = 1.27 \text{ mH}$
 $X_C = \frac{1}{2\pi fC}, C = \frac{1}{2\pi fX_C} = \frac{1}{2\pi(5 \text{ kHz})(40 \Omega)} = 0.796 \mu\text{F}$

f. $BW = \frac{f_s}{Q_s} = \frac{5 \text{ kHz}}{20} = 250 \text{ Hz}$

g. $f_2 = f_s + \frac{BW}{2} = 5 \text{ kHz} + \frac{0.25 \text{ kHz}}{2} = 5.125 \text{ kHz}$
 $f_1 = f_s - \frac{BW}{2} = 5 \text{ kHz} - \frac{0.25 \text{ kHz}}{2} = 4.875 \text{ kHz}$

4. a. $f_s = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_s)^2 C} = \frac{1}{(2\pi 1.8 \text{ kHz})^2 2 \mu\text{F}} = 3.91 \text{ mH}$

b. $X_L = 2\pi fL = 2\pi(1.8 \text{ kHz})(3.91 \text{ mH}) = 44.2 \Omega$
 $X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(1.8 \text{ kHz})(2 \mu\text{F})} = 44.2 \Omega$
 $X_L = X_C$

c. $E_{\text{rms}} = (0.707)(20 \text{ mV}) = 14.14 \text{ mV}$
 $I_{\text{rms}} = \frac{E_{\text{rms}}}{R} = \frac{14.14 \text{ mV}}{4.7 \Omega} = 3.01 \text{ mA}$

d. $P = I^2 R = (3.01 \text{ mA})^2 4.7 \Omega = 42.58 \mu\text{W}$

e. $S_T = P_T = 42.58 \mu\text{VA}$

f. $F_p = 1$

$$g. \quad Q_s = \frac{X_L}{R} = \frac{44.2 \, \Omega}{4.7 \, \Omega} = 9.4$$

$$BW = \frac{f_s}{Q_s} = \frac{1.8 \, \text{kHz}}{9.4} = 191.49 \, \text{Hz}$$

$$h. \quad f_2 = \frac{1}{2\pi} \left[\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L} \right)^2 + \frac{4}{LC}} \right]$$

$$= \frac{1}{2\pi} \left[\frac{4.7 \, \Omega}{2(3.91 \, \text{mH})} + \frac{1}{2} \sqrt{\left(\frac{4.7 \, \Omega}{3.91 \, \text{mH}} \right)^2 + \frac{4}{(3.91 \, \text{mH})(2 \, \mu\text{F})}} \right]$$

$$= \frac{1}{2\pi} [601.02 + 11.324 \times 10^3]$$

$$= 1897.93 \, \text{Hz}$$

$$f_1 = \frac{1}{2\pi} \left[-\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L} \right)^2 + \frac{4}{LC}} \right]$$

$$= \frac{1}{2\pi} [-601.02 + 11.324 \times 10^3]$$

$$= 1.707 \, \text{kHz}$$

$$P_{\text{HPF}} = \frac{1}{2} P_{\text{max}} = \frac{1}{2} (42.58 \, \mu\text{W}) = 21.29 \, \mu\text{W}$$