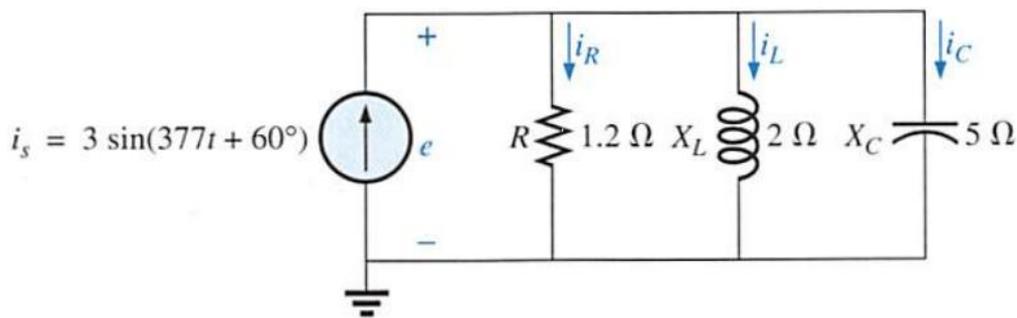


## TEST 3

Q1

For the circuit of Fig. 15.143:


- a. Find the total admittance  $\mathbf{Y}_T$  in polar form.
- b. Draw the admittance diagram.
- c. Find the value of  $C$  in microfarads and  $L$  in henries.
- d. Find the voltage  $\mathbf{E}$  and currents  $\mathbf{I}_R$ ,  $\mathbf{I}_L$ , and  $\mathbf{I}_C$  in phasor form.
- e. Draw the phasor diagram of the currents  $\mathbf{I}_s$ ,  $\mathbf{I}_R$ ,  $\mathbf{I}_L$ , and  $\mathbf{I}_C$ , and the voltage  $\mathbf{E}$ .
- f. Verify Kirchhoff's current law at one node.
- g. Find the average power delivered to the circuit.
- h. Find the power factor of the circuit, and indicate whether it is leading or lagging.



**FIG. 15.143**

Q2

Using mesh analysis, determine the current  $\mathbf{I}_L$  (in terms of  $\mathbf{V}$ ) for the network of Fig. 17.65.

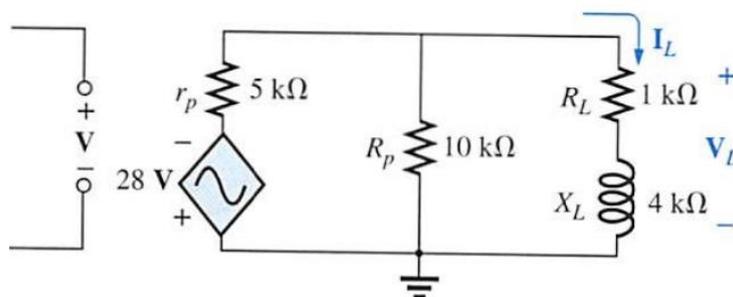

**FIG. 17.65**

Q3

- a. The bandwidth of a series resonant circuit is 200 Hz. If the resonant frequency is 2000 Hz, what is the value of  $Q_s$  for the circuit?
- b. If  $R = 2 \Omega$ , what is the value of  $X_L$  at resonance?
- c. Find the value of  $L$  and  $C$  at resonance.
- d. Find the cutoff frequencies.

Q4

- \*8. Compute the magnitude of the voltage  $E_{AB}$  for the balanced three-phase system of Fig. 23.42.

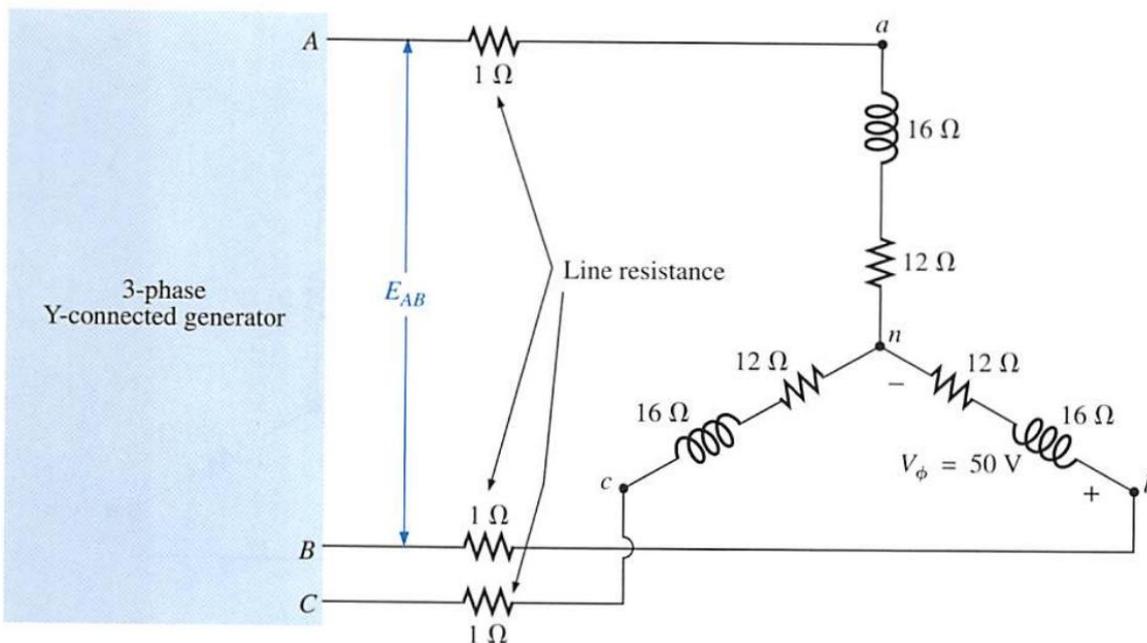


FIG. 23.42

## SOLUTION

Q1

30. a. 
$$Y_T = \frac{1}{1.2 \Omega \angle 0^\circ} + \frac{1}{2 \Omega \angle 90^\circ} + \frac{1}{5 \Omega \angle -90^\circ}$$

$$= 0.833 \text{ S} \angle 0^\circ + 0.5 \text{ S} \angle -90^\circ + 0.2 \text{ S} \angle 90^\circ$$

$$= 0.833 \text{ S} - j0.3 \text{ S} = 0.885 \text{ S} \angle -19.81^\circ$$
- b. 
$$X_C = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega X_C} = \frac{1}{(377 \text{ rad/s})(5 \Omega)} = 531 \mu\text{F}$$

$$X_L = \omega L \Rightarrow L = \frac{X_L}{\omega} = \frac{2 \Omega}{377 \text{ rad/s}} = 5.31 \text{ mH}$$
- d. 
$$E = \frac{I_s}{Y_T} = \frac{(0.707)(3 \text{ A}) \angle 60^\circ}{0.885 \text{ S} \angle -19.81^\circ} = \frac{2.121 \text{ A} \angle 60^\circ}{0.885 \text{ S} \angle -19.81^\circ} = 2.397 \text{ V} \angle 79.81^\circ$$

$$I_R = \frac{E \angle \theta}{R \angle 0^\circ} = \frac{2.397 \text{ V} \angle 79.81^\circ}{1.2 \Omega \angle 0^\circ} = 1.998 \text{ A} \angle 79.81^\circ$$

$$I_L = \frac{E \angle \theta}{X_L \angle 90^\circ} = \frac{2.397 \text{ V} \angle 79.81^\circ}{2 \Omega \angle 90^\circ} = 1.199 \text{ A} \angle -10.19^\circ$$

$$I_C = \frac{E \angle \theta}{X_C \angle -90^\circ} = \frac{2.397 \text{ V} \angle 79.81^\circ}{5 \Omega \angle -90^\circ} = 0.479 \text{ A} \angle 169.81^\circ$$
- f. 
$$I_s = I_R + I_L + I_C$$


$$2.121 \text{ A} \angle 60^\circ = 1.998 \text{ A} \angle 79.81^\circ + 1.199 \text{ A} \angle -10.19^\circ + 0.479 \text{ A} \angle 169.81^\circ$$

$$= (0.353 + j1.966) + (1.18 - j0.212) + (-0.471 + j0.086)$$

$$2.121 \text{ A} \angle 60^\circ \checkmark = 1.062 + j1.84 = 2.124 \angle 60^\circ$$
- g. 
$$P = I^2 R = (1.998 \text{ A})^2 1.2 \Omega = 4.79 \text{ W}$$
- h. 
$$F_p = \frac{G}{Y_T} = \frac{0.833 \text{ S}}{0.885 \text{ S}} = 0.941 \text{ lagging}$$

Q2

9.

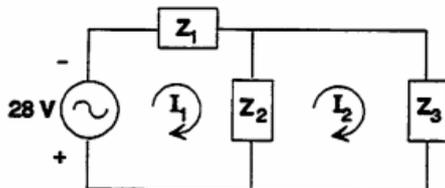

$$Z_1 = 5 \text{ k}\Omega \angle 0^\circ$$

$$Z_2 = 10 \text{ k}\Omega \angle 0^\circ$$

$$Z_3 = 1 \text{ k}\Omega + j4 \text{ k}\Omega = 4.123 \text{ k}\Omega \angle 75.96^\circ$$

$$I_1(Z_1 + Z_2) - Z_2 I_2 = -28 \text{ V}$$

$$I_2(Z_2 + Z_3) - Z_2 I_1 = 0$$

$$\begin{array}{r} (Z_1 + Z_2)I_1 - Z_2 I_2 = -28 \text{ V} \\ -Z_2 I_1 + (Z_2 + Z_3)I_2 = 0 \end{array}$$

$$I_L = I_2 = \frac{-Z_2 28 \text{ V}}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} = -3.165 \times 10^{-3} \text{ V} \angle 137.29^\circ$$

Q3

7. a.  $BW = \frac{f_s}{Q_s} \Rightarrow Q_s = f_s/BW = 2000 \text{ Hz}/200 \text{ Hz} = 10$
- b.  $Q_s = \frac{X_L}{R} \Rightarrow X_L = Q_s R = (10)(2 \Omega) = 20 \Omega$
- c.  $L = \frac{X_L}{2\pi f} = \frac{20 \Omega}{(6.28)(2 \text{ kHz})} = 1.59 \text{ mH}$   
 $C = \frac{1}{2\pi f X_C} = \frac{1}{(6.28)(2 \text{ kHz})(20 \Omega)} = 3.98 \mu\text{F}$
- d.  $f_2 = f_s + BW/2 = 2000 \text{ Hz} + 100 \text{ Hz} = 2100 \text{ Hz}$   
 $f_1 = f_s - BW/2 = 2000 \text{ Hz} - 100 \text{ Hz} = 1900 \text{ Hz}$

Q4

8.  $Z_\phi = 12 \Omega + j16 \Omega = 20 \Omega \angle 53.13^\circ$   
 $I_\phi = \frac{V_\phi}{Z_\phi} = \frac{50 \text{ V}}{20 \Omega} = 2.5 \text{ A}$   
 $Z_{T_\phi} = 13 \Omega + j16 \Omega = 20.62 \Omega \angle 50.91^\circ$   
 $V_\phi = I_\phi Z_{T_\phi} = (2.5 \text{ A})(20.62 \Omega) = 51.55 \text{ V}$   
 $V_L = \sqrt{3} V_\phi = (\sqrt{3})(51.55 \text{ V}) = 89.285 \text{ V}$