

Test 1 – Circuit Analysis

Question 1 (parallel and series network)

7.5 For the network shown in Fig. 7.67: (a) Determine R_T ; (b) Find I_s , I_1 , and I_2 ; (c) Find V_a


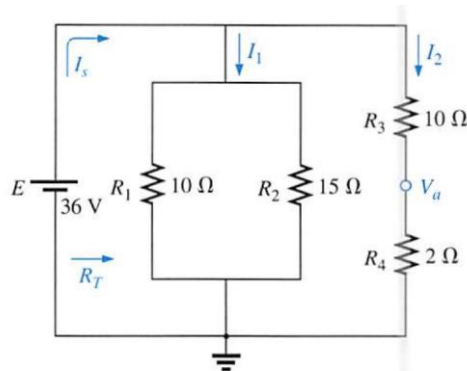


FIG. 7.67
Problem 5.

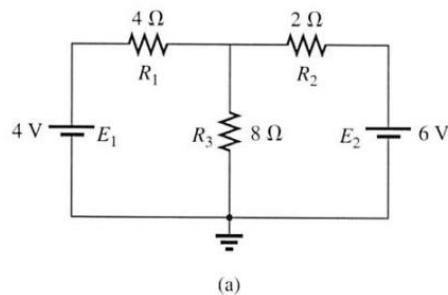Question 2 (mesh analysis)


8-12-a Using mesh analysis (KVL), find the magnitude and direction of the current through each of the resistor, for the circuit shown below.



(a)
Fig 8.102

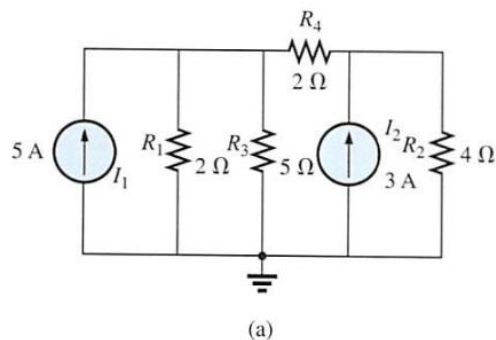Question 3 (nodal analysis)

8-32-a Write nodal equations for the circuit shown below, and solve for all the nodal voltage points.



(a)
Fig 8.111.a

Question 4 (Superposition Theorem)

9-3-a Using Superposition Theorem, Find the current through R_1 .

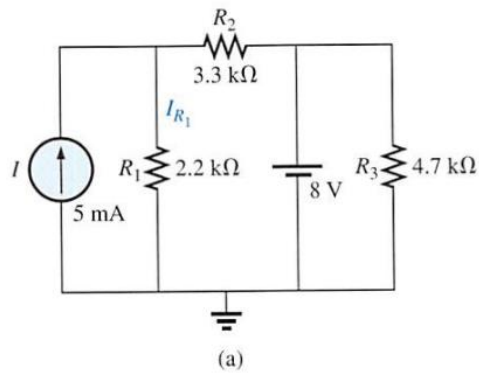


Fig. 9.127

Question 5 (Thevenin Theorem)

9-7-a Find the Thevenin equivalent circuit for the network external to the resistor R , in the figure shown below.

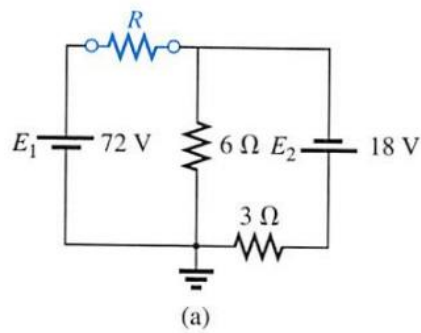


Fig. 9.131