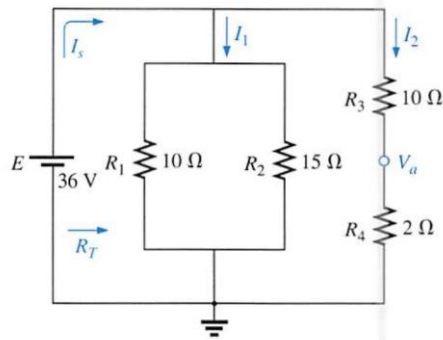


## Test 1 – Circuit Analysis

### Question 1 (parallel and series network)


7.5 For the network shown in Fig. 7.67: (a) Determine  $R_T$ ; (b) Find  $I_s$ ,  $I_1$ , and  $I_2$ ; (c) Find  $V_a$



**FIG. 7.67**  
Problem 5.
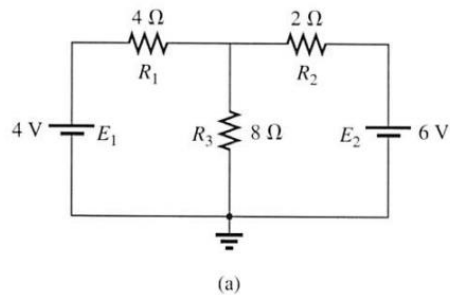
### Question 2 (mesh analysis)


8-12-a Using mesh analysis (KVL), find the magnitude and direction of the current through each of the resistor, for the circuit shown below.



(a)  
Fig 8.102
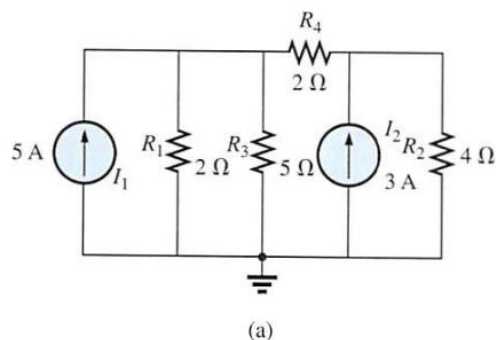
### Question 3 (nodal analysis)

8-32-a Write nodal equations for the circuit shown below, and solve for all the nodal voltage points.



(a)

Fig 8.111.a

Question 4 (Superposition Theorem)

9-3-a Using Superposition Theorem, Find the current through  $R_1$ .

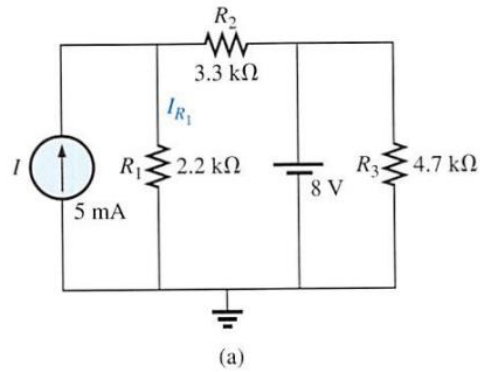


Fig. 9.127

Question 5 (Thevenin Theorem)

9-7-a Find the Thevenin equivalent circuit for the network external to the resistor  $R$ , in the figure shown below.

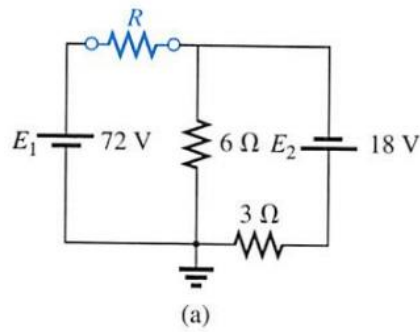



Fig. 9.131

Solution

Question 1

5. a.  $R' = R_1 \parallel R_2 = 10 \Omega \parallel 15 \Omega = 6 \Omega$   
 $R_T = R' \parallel (R_3 + R_4) = 6 \Omega \parallel 12 \Omega = 4 \Omega$
- b.  $I_s = \frac{E}{R_T} = \frac{36 \text{ V}}{4 \Omega} = 9 \text{ A}, I_1 = \frac{E}{R'} = \frac{36 \text{ V}}{6 \Omega} = 6 \text{ A}$   
 $I_2 = \frac{E}{R_3 + R_4} = \frac{36 \text{ V}}{12 \Omega} = 3 \text{ A}$
- c.  $V_a = I_2 R_4 = (3 \text{ A})(2 \Omega) = 6 \text{ V}$


Question 2

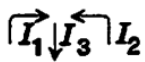12. a.  
$$\begin{aligned} 4 - 4I_1 - 8I_3 &= 0 \\ 6 - 2I_2 - 8I_3 &= 0 \\ I_1 + I_2 &= I_3 \end{aligned}$$

---


$$I_1 = -\frac{1}{7} \text{ A}, I_2 = \frac{5}{7} \text{ A}, I_3 = \frac{4}{7} \text{ A}$$
$$I_{R_1} = I_1 = -\frac{1}{7} \text{ A}, I_{R_2} = I_2 = \frac{5}{7} \text{ A}, I_{R_3} = I_3 = \frac{4}{7} \text{ A}$$

Question 3


32. a. 
$$V_1 \left[ \frac{1}{2} + \frac{1}{5} + \frac{1}{2} \right] - \frac{1}{2} V_2 = 5 \quad \begin{aligned} V_1 &= 8.077 \text{ V} \\ V_2 &= 9.385 \text{ V} \end{aligned}$$
$$V_2 \left[ \frac{1}{2} + \frac{1}{4} \right] - \frac{1}{2} V_1 = 3$$

Question 4

3. a.

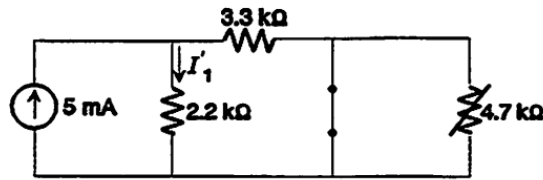
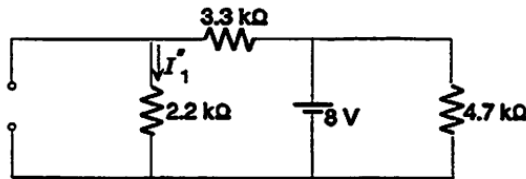
$$I_1 = \frac{3.3 \text{ k}\Omega (5 \text{ mA})}{2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega} = \frac{16.5 \text{ mA}}{5.5} = 3 \text{ mA}$$




$$I''_1 = \frac{8 \text{ V}}{3.3 \text{ k}\Omega + 2.2 \text{ k}\Omega} = \frac{8 \text{ V}}{5.5 \text{ k}\Omega} = 1.4545 \text{ mA}$$

$$I_1 = I'_1 + I''_1 = 3 \text{ mA} + 1.4545 \text{ mA} = 4.4545 \text{ mA}$$


Question 5

7. (I):  $R_{Th}$ :

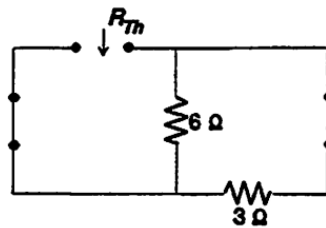

$$R_{Th} = 6 \Omega \parallel 3 \Omega = 2 \Omega$$

$E_{Th}$ :

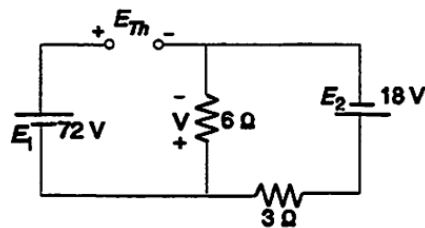

$$V = \frac{6 \Omega (18 \text{ V})}{6 \Omega + 3 \Omega} = 12 \text{ V}$$

$$E_{Th} = 72 \text{ V} + V = 84 \text{ V}$$